

# Coupling factors of a 3-winding transformer


Arno Buij

When two of the coupling factors of the 3-winding transformer shown here are known, the third is confined to a certain range. How to find that range?  
For winding 1 of the transformer we have the equation:

$$V_1 = j\omega.(L_1 I_1 + M_{12} I_2 + M_{13} I_3)$$

where  $V_1$  is the voltage across winding 1,  
 $L_1$  is the open circuit inductance of winding 1,  
 $\omega$  is the frequency of a sinusoidal current,  
 $I_j$  are the winding currents and

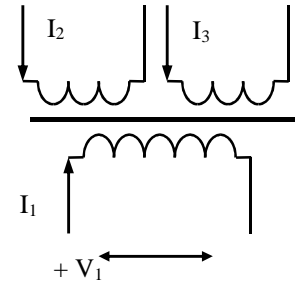$M_{ij}$  are the mutual inductances between the windings:  $M_{i,j} = k_{i,j}\sqrt{L_i L_j}$ .



Scaling the currents  $I_j$  to the open circuit inductances of their windings and to the frequency as:  $i_j = j\omega I_j \sqrt{L_j}$

and scaling the voltages  $V_i$  likewise as:  $v_i = \frac{V_i}{\sqrt{L_i}}$ ,

the behaviour of the transformer can now be described by means of a coupling matrix  $K$ , where  $\underline{v} = K \cdot \underline{i}$ , as follows:

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & k_{12} & k_{13} \\ k_{12} & 1 & k_{23} \\ k_{13} & k_{23} & 1 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

To find the currents in all windings we have to solve the equation:  $\underline{i} = K^{-1} \cdot \underline{v}$ .

Example: for finding short-circuit currents in windings 2 and 3 with a voltage present at winding 1 we can write:  $v_1=1, v_2=0, v_3=0$  and calculate  $\underline{i}$ .

This requires matrix inversion and a non-zero determinant  $D$  of matrix  $K$ :

$$D = [1 - k_{12}^2 - k_{13}^2 - k_{23}^2 + 2k_{12}k_{13}k_{23}]$$

Physically valid situations must have  $D > 0$ .

(Example: when all values of  $k$  are 0.9 we have  $D = 0.028$ ).

The determinant gives a criterion for the third coupling factor when the first two are given. Let  $k_{12}$  and  $k_{13}$  be given. A valid range for  $k_{23}$  can then be found by solving the second order equation for  $D = 0$ .

The two solutions are:

$$k_{23, \min, \max} = k_{12}k_{13} \pm \sqrt{k_{12}^2 k_{13}^2 - k_{12}^2 - k_{13}^2 + 1}$$

A special case is  $k_{12} = k_{13} = k_1$  and  $k_{23} = k_2$ . This leads to:

$$k_{2, \min} = 2(k_1)^2 - 1 \text{ and obviously: } k_{2, \max} = 1$$

Example: a transformer has a primary winding 1 and two equal secondary windings 2 and 3. Let  $k_1 = 0.9$ . The coupling factor between the secondary windings must satisfy:  
 $1 > k_2 > 0.62$ .

Note that a zero coupling factor  $k_2$  is only possible if  $k_1 < \frac{1}{2}\sqrt{2}$ .